

### Lesson plan

| <b>Name of Faculty</b>                         |            | Guest Faculty  |                      |  |
|--|------------|--|----------------------|--|
| <b>Discipline</b>                              |            | Electrical Engineering   |                      |  |
| <b>Year</b>                                    |            | 1 <sup>st</sup>  |                      |  |
| <b>Subject</b>                                 |            | Fundamental of Electrical & Electronics Engg.  |                      |  |
| <b>Lesson Plan Duration</b>                    |            | 2020-21  |                      |  |
| <b>Work load [Theory + Practical] Per Week</b> |            | [02+02]  |                      |  |
| <b>Week</b>                                    | <b>Day</b> | <b>Theory Topic/ Assignment/ Test</b>  | <b>Practical Day</b> | <b>Topic</b>   |
| 1  | 1          | <b>1 Overview of DC Circuits</b>   | Day 1                | Operation and use of electrical measuring instruments and other accessories  |
|  | 2          | Simple problems on series and parallel combination of resistor and capacitors  |                      |  |
| 2  | 1          | Kirchhoff's current law and Kirchhoff's voltage law  | Day 1                | File Checking and revision   |
|  | 2          | Star – Delta connections and their conversion  |                      |  |
| 3  | 1          | <b>2 DC Circuit Theorems</b> Thevenin's theorem and problems   | Day 1                | Measurement of resistance of an ammeter and a voltmeter  |
|  | 2          | Norton's theorem and problems  |                      |  |
| 4  | 1          | Superposition nodal analysis and problems  | Day 1                | File Checking and revision   |
|  | 2          | Mesh analysis and problems   |                      |  |
| 5  | 1          | Maximum Power Transfer and problems  | Day 1                | Verification of following Theorems Thevenin's theorem  |
|  | 2          | <b>3 Voltage and Current Sources</b>   |                      |  |
| 6  | 1          | voltage source, symbol and graphical representation  | Day 1                | Norton's theorem   |
|  | 2          | characteristics of ideal and practical sources   |                      |  |
| 7  | 1          | current sources, symbol, characteristics   | Day 1                | File Checking and revision   |
|  | 2          | First Internal   |                      |  |
| 8  | 1          | <b>4 Semiconductor Physics</b> , basic atomic structure and energy levels  | Day 1                | First Internal evaluation  |
|  | 2          | concept of insulators, conductors and semi-conductors  |                      |  |
| 9  | 1          | structure of (Ge) and (Si) covalent bonds, Intrinsic, extrinsic semiconductor and doping                               | Day 1                | Observation of change in resistance of a bulb in hot and cold conditions, using voltmeter and ammeter  |
|  | 2          | Energy level diagram of conductor, insulator and semiconductor   |                      |  |
| 10   | 1          | P and N type semiconductors and their conductivity, effect of temperature  | Day 1                | File Checking and revision   |
|  | 2          | <b>5 Semiconductor Diode</b> , PN junction diode, forward and reverse biased PN junction, drift and diffusion currents |                      |  |
| 11   | 1          | V-I characteristics, static and dynamic resistance   | Day 1                | Verification of Kirchhoff's Current and Voltage Laws in a dc circuit   |
|  | 2          | Application of diode as half-wave, full wave and bridge rectifiers   |                      |  |
| 12   | 1          | Peak Inverse Voltage, rectification efficiencies and ripple factor calculations  | Day 1                | File Checking and revision   |
|  | 2          | shunt capacitor filter, series inductor filter, LC and $\pi$ filters   |                      |  |
| 13   | 1          | Types of diodes, characteristics and applications of Zener diodes  | Day 1                | To find the ratio of inductance of a coil having air-core and iron-core respectively and to observe the effect of introduction of a magnetic core on coil inductance |
|  | 2          | Revision of syllabus / Second Internal   |                      |  |
| 14   | 1          | <b>6 Electro Magnetic Induction</b> , flow of electric current, magnetic circuit, concept (MMF)                        | Day 1                | File Checking and revision   |
|  | 2          | flux, reluctance, permeability, analogy between electric and magnetic circuit  |                      |  |
|  | 1          | Faraday's laws of electro-magnetic induction   | Day 1                | Second Internal evaluation   |

|    |   |  |       |   |
|----|---|--|-------|---|
| 15 | 2 | self and mutual induction, self and mutually induced e.m.f simple numerical problems                                       |       |   |
| 16 | 1 | current growth, decay and time constant in an inductive (RL) circuit   | Day 1 | Charging and testing of a lead - acid storage battery   |
|    | 2 | Energy stored in an inductor, series and parallel combination of inductors   |       |   |
| 17 | 1 | <b>7 Batteries</b> Basic idea of primary and secondary cells Construction, working principle and applications of Lead-Acid | Day 1 | File Checking and revision  |
|    | 2 | Nickel-Cadmium and Silver-Oxide batteries  |       |   |
| 18 | 1 | Charging methods used for lead-acid battery (accumulator), Care and maintenance of lead-acid battery                       | Day 1 | Measurement of power and power factor in a single phase RLC circuit and calculation of active and reactive powers in the circuit. |
|    | 2 | Series and parallel connections of batteries, General idea of solar cells,   |       |   |
| 19 | 1 | solar panels and their applications, Introduction to maintenance free batteries  | Day 1 | Plotting of V-I characteristics of a PN junction diode & Zener diode  |
|    | 2 | <b>8 AC Fundamentals</b> ,Concept of alternating quantities , Difference between ac and dc                                 |       |   |
| 20 | 1 | Concepts of: cycle, frequency, time period, amplitude, instantaneous value   | Day 1 | File Checking and revision  |
|    | 2 | average value, r.m.s. value,   |       |   |
| 21 | 1 | Maximum value, form factor and peak factor.  | Day 1 | Observe the output of waveform using<br>a.) Half-wave rectifier circuit using one diode   |
|    | 2 | Representation of sinusoidal quantities by phasor diagrams.  |       |   |
| 22 | 1 | Equation of sinusoidal wave form for an alternating quantity and its derivation  | Day 1 | b.) Full-wave rectifier circuit using two diodes  |
|    | 2 | Effect of alternating voltage applied to a pure resistance   |       |   |
| 23 | 1 | Pure inductance and pure capacitance.  | Day 1 | c.) Bridge-rectifier circuit using four diodes  |
|    | 2 | <b>9 AC Circuits</b> , Concept of inductive and capacitive reactance   |       |   |
| 24 | 1 | Alternating voltage applied to resistance and inductance in series.  | Day 1 | File Checking and revision  |
|    | 2 | Alternating voltage applied to resistance and inductance in series.  |       |   |
| 25 | 1 | Introduction to series and parallel resonance and its conditions   | Day 1 | Plotting of the wave shape of full wave rectifier with<br>a. Shunt capacitor filter   |
|    | 2 | Power in pure resistance, inductance and capacitance, power in combined RLC circuits                                       |       |   |
| 26 | 1 | Power factor, active and reactive power and their significance, definition and significance of power factor                | Day 1 | b. Series inductor filter   |
|    | 2 | Definition of conductance, susceptance, admittance, impedance and their units  |       |   |
| 27 | 1 | <b>10 Introduction to Bipolar-Transistors</b> PNP and NPN transistors , CB and CE and CC configurations                    | Day 1 | File Checking and revision  |
|    | 2 | Comparison of CB, CE and CC Configurations   |       |   |
| 28 | 1 | Transistor as an amplifier in CE Configuration   | Day 1 | Plotting of input and output characteristics and calculation of parameters of transistors in CE configuration                     |
|    | 2 | concept of DC load line and calculation of current gain and voltage gain using DC load line                                |       |   |
| 29 | 1 | <b>11 Transistor Biasing Circuits</b> , Concept of transistor biasing and selection of operating point                     | Day 1 | File Checking and revision  |
|    | 2 | Need for stabilization of operating point. Different types of biasing circuits.  |       |   |
|    | 1 | <b>12 Field Effect Transistors</b> , Construction,   | Day 1 | Plotting of input and output  |

|    |   |  |       |  |
|----|---|--|-------|--|
| 30 |   | operation and characteristics  |       | characteristics and calculation of parameters of transistors in CB configuration |
|    | 2 | Construction, operation and characteristics of a MOSFET in depletion and enhancement modes                                 |       |  |
| 31 | 1 | CMOS - advantages and applications   | Day 1 | File Checking and revision   |
|    | 2 | Comparison of JFET, MOSFET and BJT   |       |  |
| 32 | 1 | <b>13 Introduction to Electrical Machines</b><br>Principal of operation, construction of Transformers                      | Day 1 | Plotting of V-I characteristics of a FET   |
|    | 2 | single phase transformer, turns ratio , efficiency, loses in a transformer   |       |  |
| 33 | 1 | Principal of operation, construction of DC motor and generator, Characteristics of different types of DC machines, Starter | Day 1 | To determine the efficiency of single phase Transformer                          |
|    | 2 | AC machines : Principal and working of synchronous machines  |       |  |
| 34 | 1 | Single phase induction motor   | Day 1 | File Checking and revision   |
|    | 2 | Revision and final assessment  |       |  |
| 35 | 1 | Revision/Hsbte Old Question Paper  | Day 1 | Final evaluation   |
|    | 2 | Revision/Hsbte Old Question Paper  |       |  |