Example 2.15. Draw the wiring diagram for a residential house. The circuit should consider the separate panels for lighting and power controls. Draw the circuit starting from energy main switch etc. Show at least four subcircuits on each lighting and power circuits. Solution.



Fig. 2.47 : Wiring diagram

Example 2.21. Draw the wiring diagram of fluorescent tube controlled from one s Solution.



Fig. 2.60 : Wiring diagram of fluorescent tube light







Fig. 2.65 : Installation plan



Fig. 2.66 : Installation plan in 3D view

Panels/ Distribution Boards



Fig. 2.67 : Schematic diagram



Fig. 2.68 : Wiring diagram

Example 2.27. The plan of a two room set is shown in fig. 2.69 below. Draw the installation plan and wiring diagram for doing wiring of the rooms. Assume the height of the roof is 3.5 m. One plug point is to be provided in each room.



Fig. 2.69 : Plan of the House

59

ISHAN'S Electrical Engineering Design and _{Draw} **Solution.** The installation plan for doing wiring of the rooms shown in fig. 2.70 is sh_{0} Fig. 2.70 below.







Fig. 2.71 : Installation plan in 3D view

60



Example 2.28. The plan of a two room set consisting of a room of size $4m \times 4m$ and a store of size $2m \times 4m$ is drawn in fig. 2.74 below. Draw the installation and wiring diagram.



Fig. 2.74 : Plan of Two Room Set

Example 2.30. Draw the single line diagram showing electrical connection to two no. 3 phase motors. The circuit should consists of energymeter, main switch, starters etc.



Fig. 2.79 : Single Line Diagram

Example 2.31. Power supply to a 3phase 10 H.P induction motor is to be given which is installed in a room of size $6m \times 5$ m high. The motor is one meter away from the wall. Draw the installation plan and wiring diagram showing locations of energymeter, main switch, 3ϕ induction motor etc.

Students does not confused among 400V, 415V, 440V in 3- ϕ system. India standard voltage in 3- ϕ system is 400V. (Because 230V × $\sqrt{3} = 400$ V) $_{40V}$ voltage drop in lines actually our line voltage is 415V. Write on body of 2 1 phase equipment design for Higher voltage than actual *i.e.* 440V. 50, 415/440V s/ Distribution Boards

Solution.

1





EXERCISE